



Welcome to The Logic Design Lab!

Fall 2021


Lab 4: Finite State Machines

Prof. Chun-Yi Lee

Department of Computer Science
National Tsing Hua University

Agenda

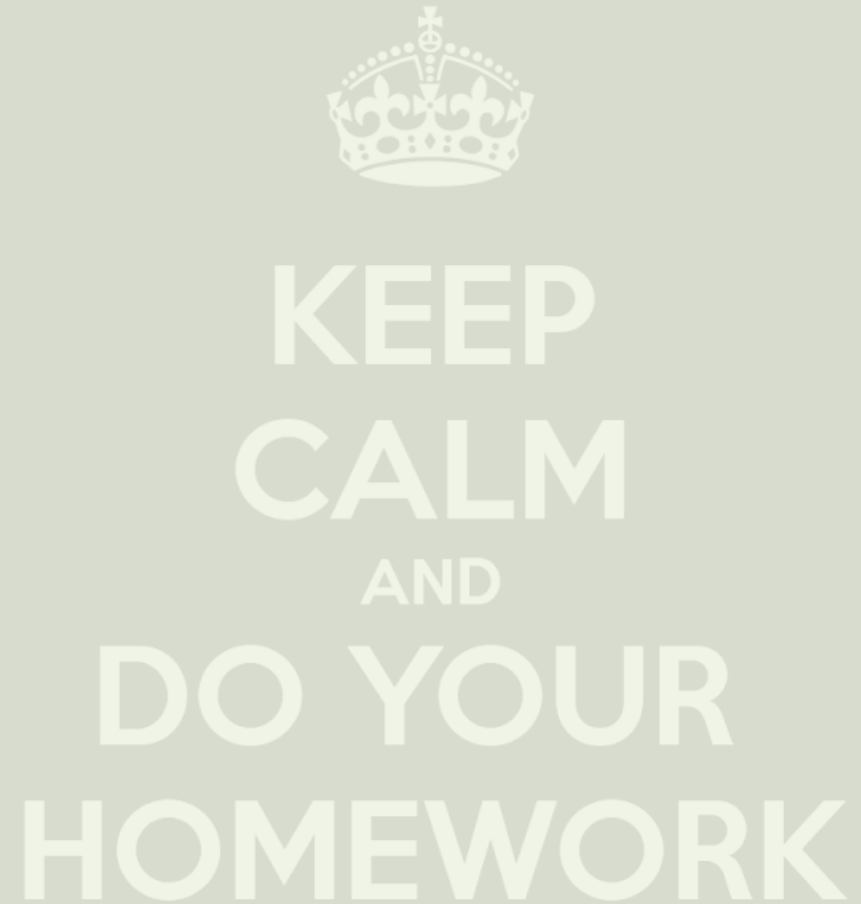- Lab 4 Outline
- Lab 4 Basic Questions
- Lab 4 Advanced Questions



Lab 4 Outline

- Basic questions (1.5%)
 - Individual assignment
 - Due on **11/2/2021 (Thu). In class.**
- Advanced questions (5%)
 - Group assignment
 - Demonstration on your FPGA board (**In class**)
 - Assignment submission (**Submit to eeclass**)
 - ILMS submission due on **11/11/2021 (Thu). 23:59:59.**
 - Source codes and testbenches
 - Lab report in PDF

Lab 4 Rules

- Please note that grading will be based on **NCVerilog**
- You can use **ANY** modeling techniques
- If not specifically mentioned, we assume the following SPEC
 - **clk** is **positive edge triggered**
 - Synchronously reset the Flip-Flops when **rst_n == 1'b0**, if there **exists one rst_n signal in the specification**

Lab 4 Submission Requirements

- Source codes and testbenches
 - Please follow the templates **EXACTLY**
 - We will test your codes by TAs' testbenches
- Lab 4 report
 - Please submit your report in a single **PDF** file
 - Please **draw** the **block diagrams** and **state transition diagrams** of your designs
 - Please **explain** your designs in detail
 - Please **list** the contributions of each team member clearly
 - **Please explain how you test your design**
 - What you have **learned** from Lab 4

Agenda

- Lab 4 Outline
- **Lab 4 Basic Questions**
- Lab 4 Advanced Questions




Basic Questions

- Individual assignment
- Verilog questions (due on 11/2/2021. In class.)
 - Moore machine
 - Mealy machine
 - Many-to-one linear-feedback shift register
 - One-to-many linear-feedback shift register
- Demonstrate your work by waveforms

Verilog Basic Question 1

- Moore machine
 - **Green** represents input, while **red** represents output
 - Output your **current state** as well
 - When **rst_n == 1'b0**, **state** = S0


Moore

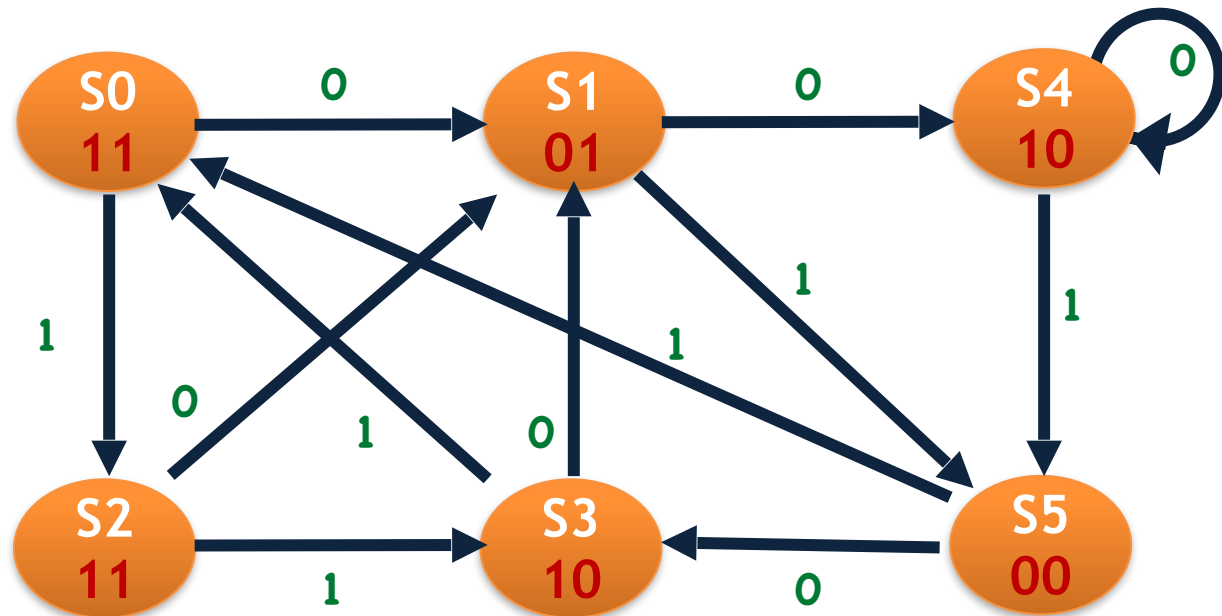

S0: 3'b000 S1: 3'b001 S2: 3'b010 S3: 3'b011 S4: 3'b100 S5: 3'b101

Verilog Basic Question 2

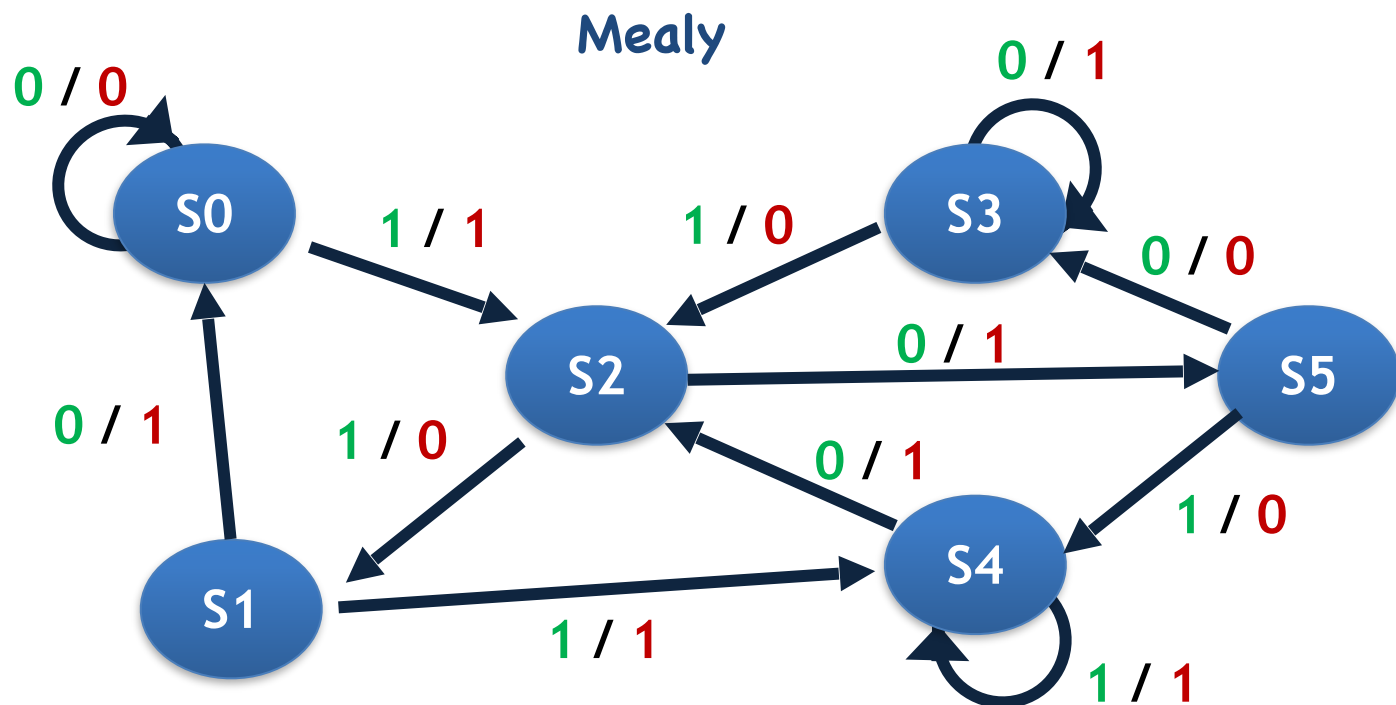
- Mealy machine
 - **Green** represents input, while **red** represents output
 - Output your **current state** as well
 - When `rst_n == 1'b0`, `state = S0`



S0: 3'b000 S1: 3'b001 S2: 3'b010 S3: 3'b011 S4: 3'b100 S5: 3'b101

Verilog Basic Question 3

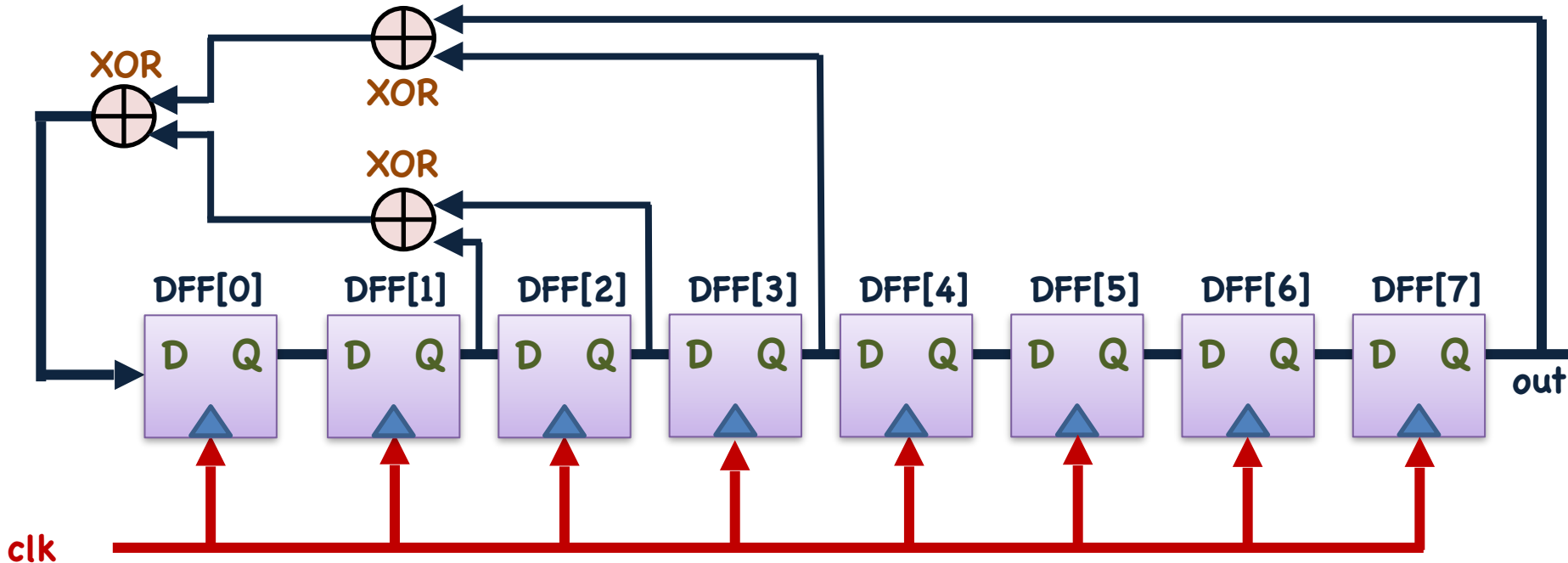
- Many-to-one linear-feedback shift register (LFSR)



- When `rst_n == 1'b0`, reset DFF[7:0] to `8'b10111101`
- Please draw the **state transition diagram** of the DFFs in LFSR for the first ten states after `rst_n` is raised to `1'b1` in your report
- Please describe what happens if we reset the DFFs to `8'd0` in your report

Verilog Basic Question 4

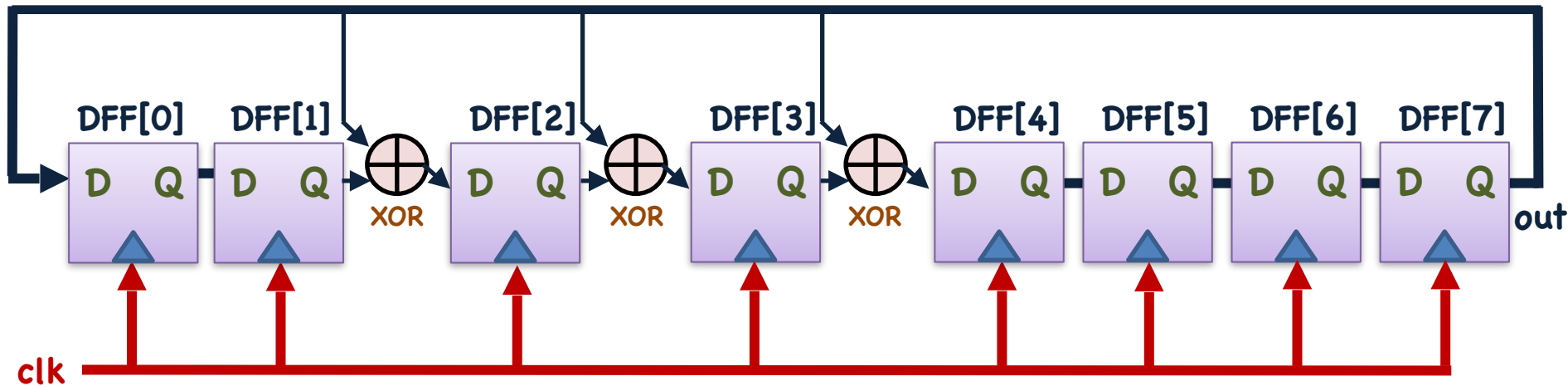- One-to-many linear-feedback shift register (LFSR)



- When `RESET == 1'b0`, reset DFF[7:0] to `8'b10111101`
- Please draw the **state transition diagram** of the DFFs in LFSR for the first ten states after `rst_n` is raised to `1'b1` in your report
- Please describe what happens if we reset the DFFs to `8'd0` in your report